
A satellite with a large blue and gold antenna is shown in space, orbiting Earth. The Earth's horizon is visible at the bottom, showing blue oceans and green landmasses. The background is a dark starry sky with a crescent moon in the upper right.





***Down-conversion and Correlation
Engines for GPS Receivers***

- A Low Power Solution


GPS System

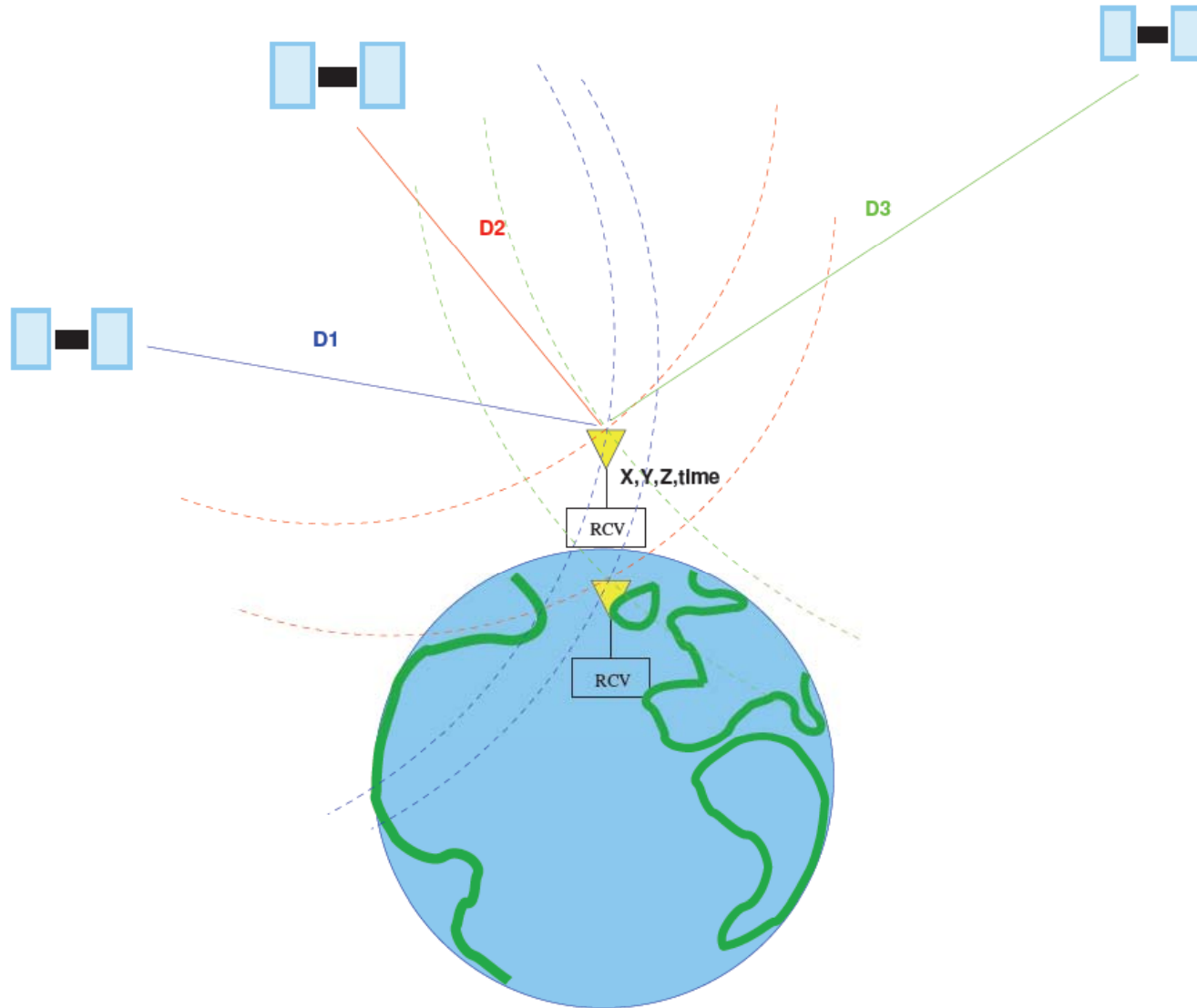

GPS Signal Processing

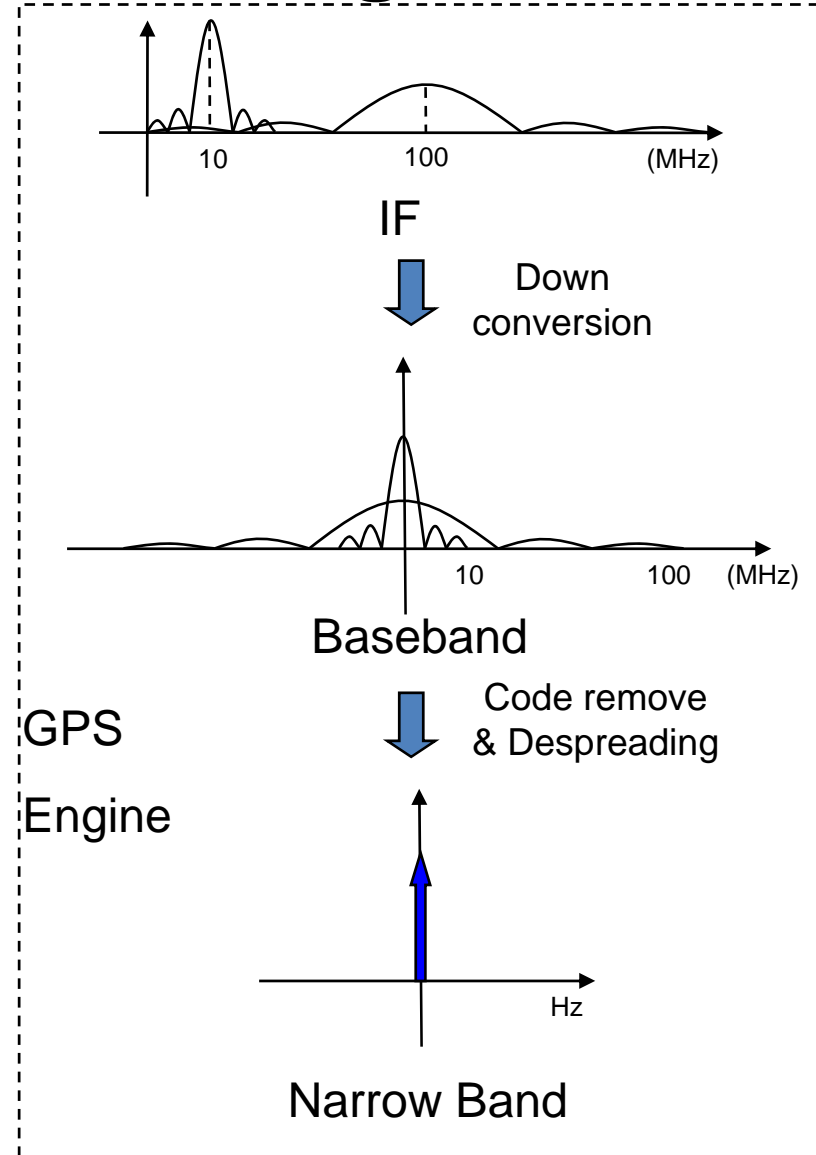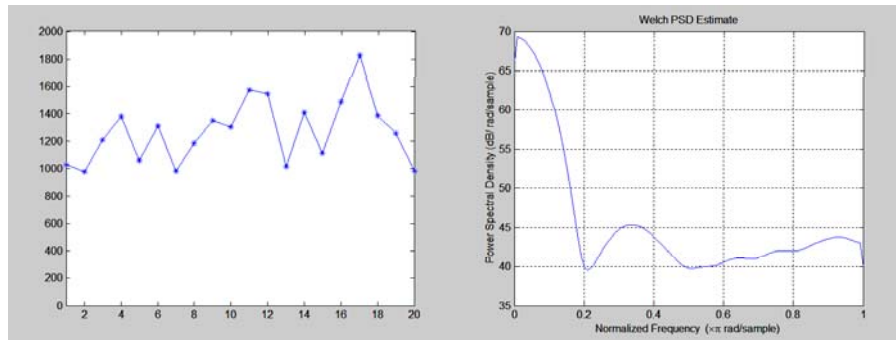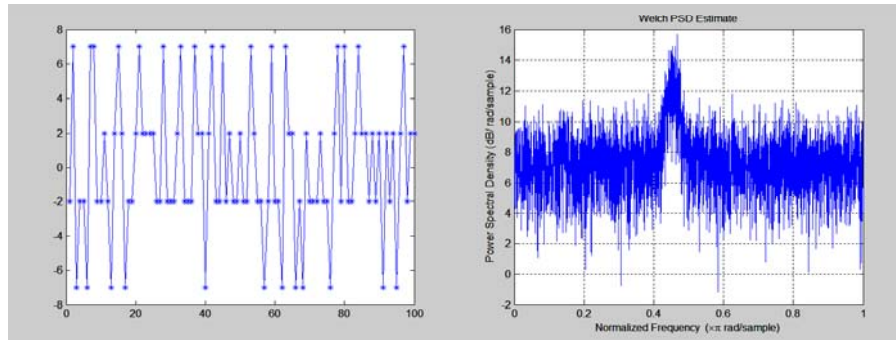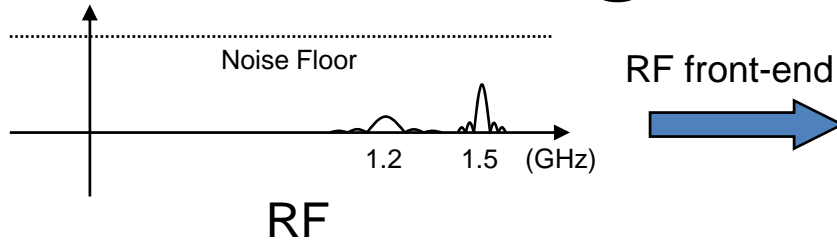

GPS Receiver

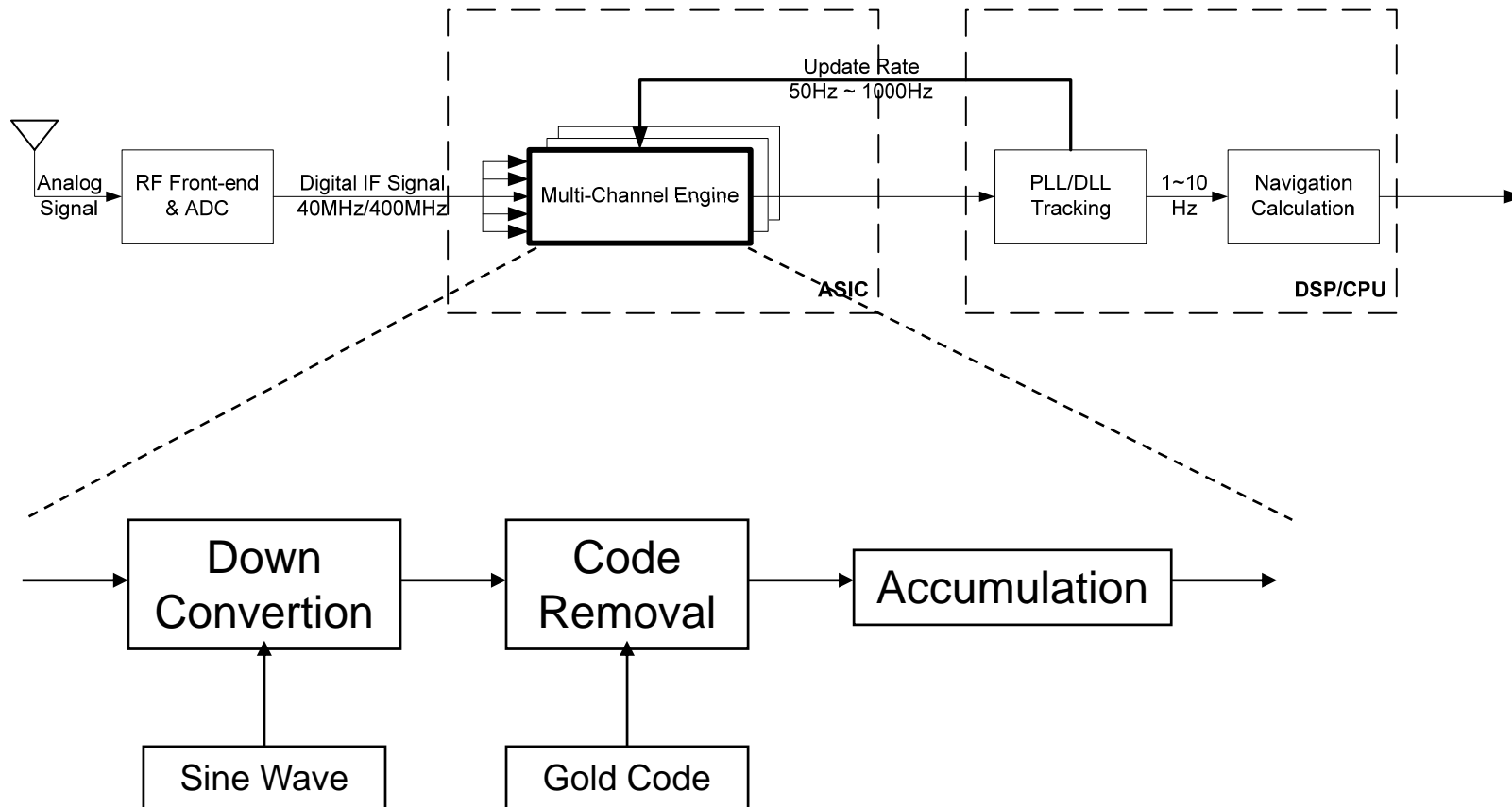

Design Process

Software Tools	Matlab	Verilog	RC Compiler	Cadence	NanoSim
Purpose	Algorithm Simulation	Circuit Design	Circuit Synthesis	Verification & Measurement	
Files Generated	Testing Vectors	Hardware Description	Synthesized Circuit	HSpice Netlist	Waveforms



A Low Power Design

$$P = CV_{DD}^2 f$$




Voltage Scaling



Pipelining?

Parallelism?

Sequential Implementation

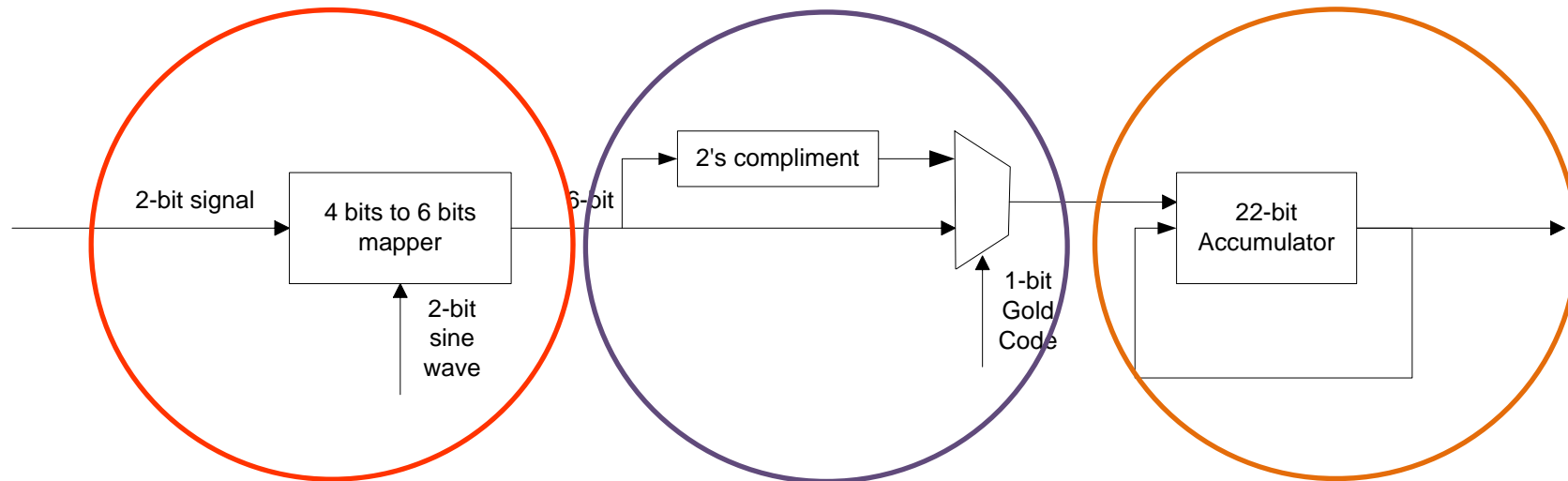


Down
Conversion

Code removal

Accumulation


Dealing with 40MHz

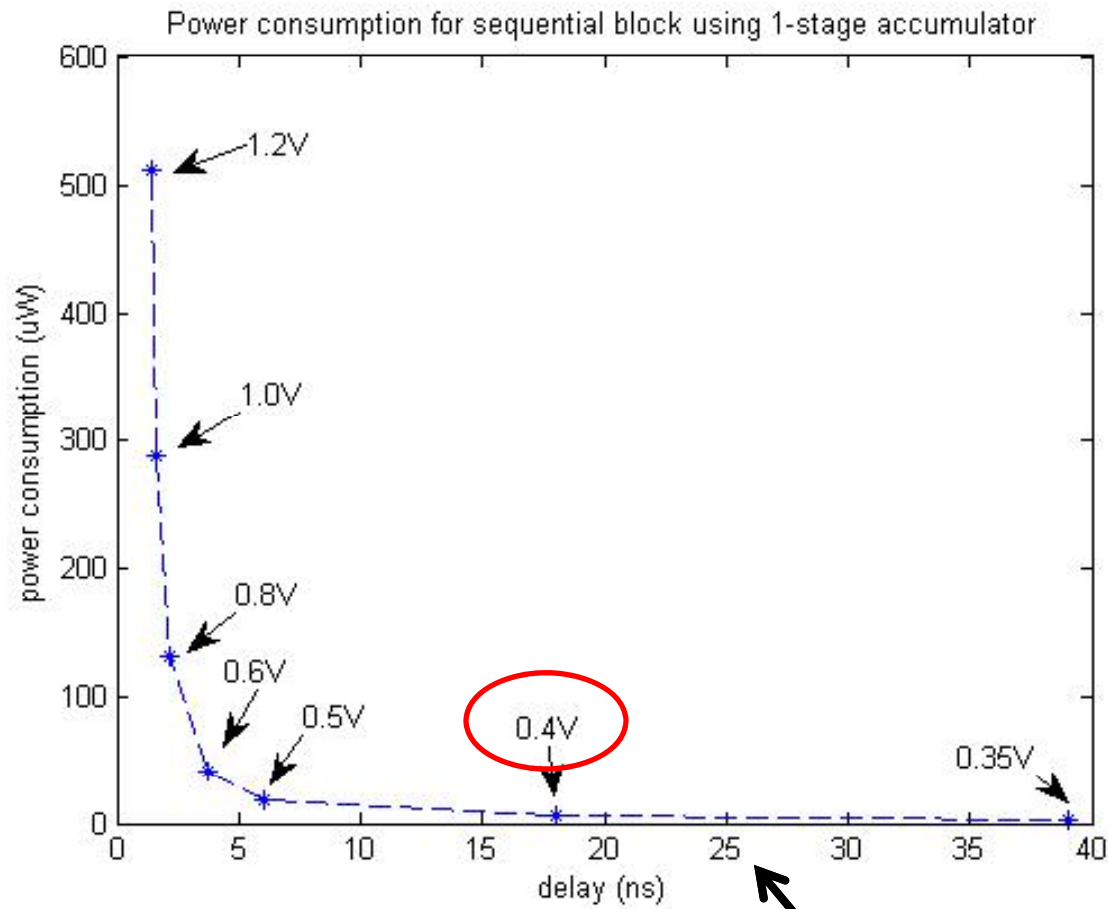

40MHz

No parallel paths needed


Reliability Problem

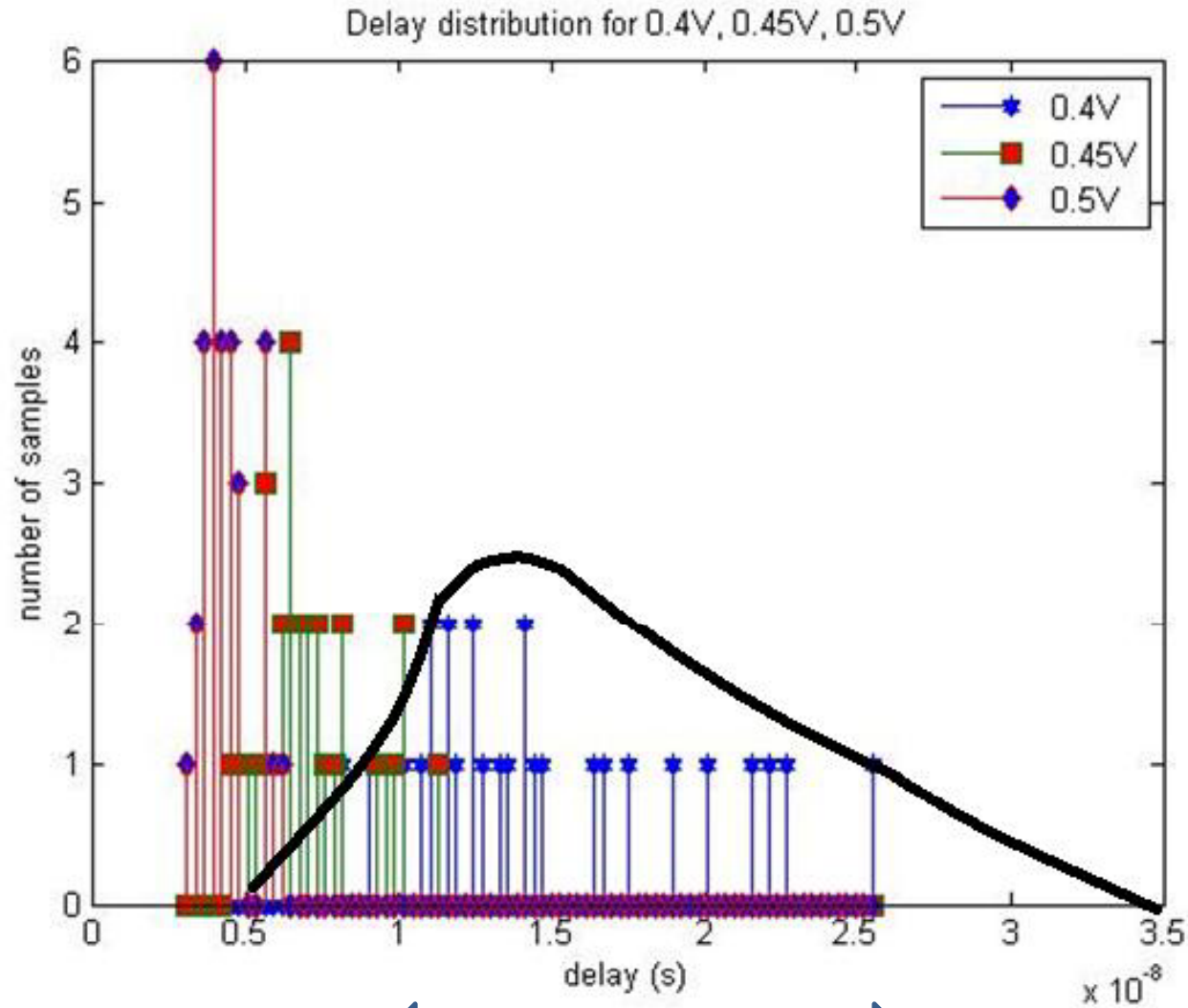


Monte Carlo

Need to
reduce
delay

Reduce whose delay?

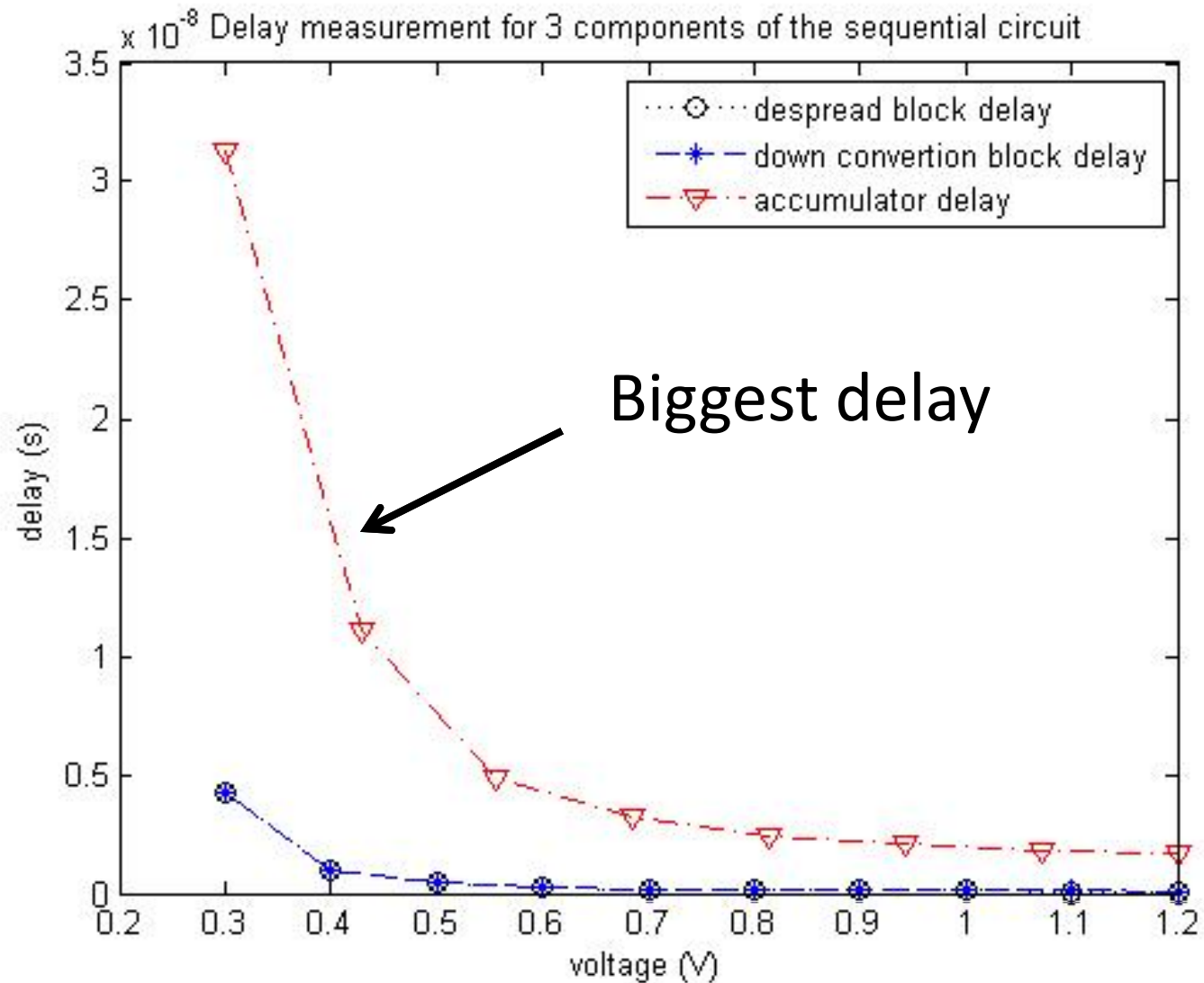


Pipeline the Accumulator!!!

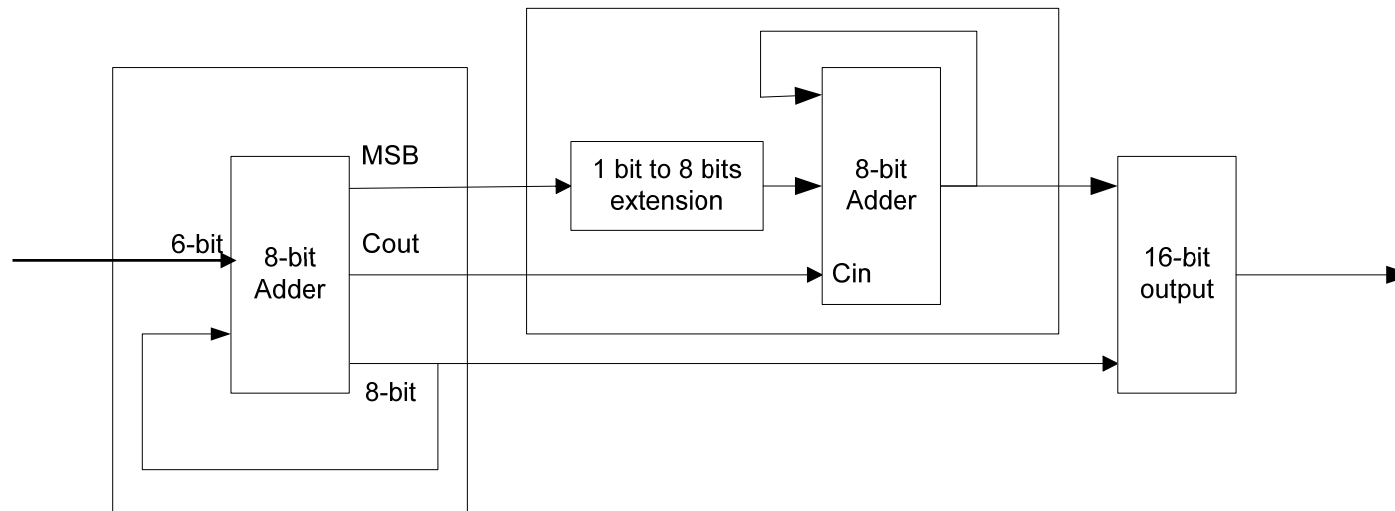

2-Stage Pipelined Accumulator

Pipeline the Accumulator

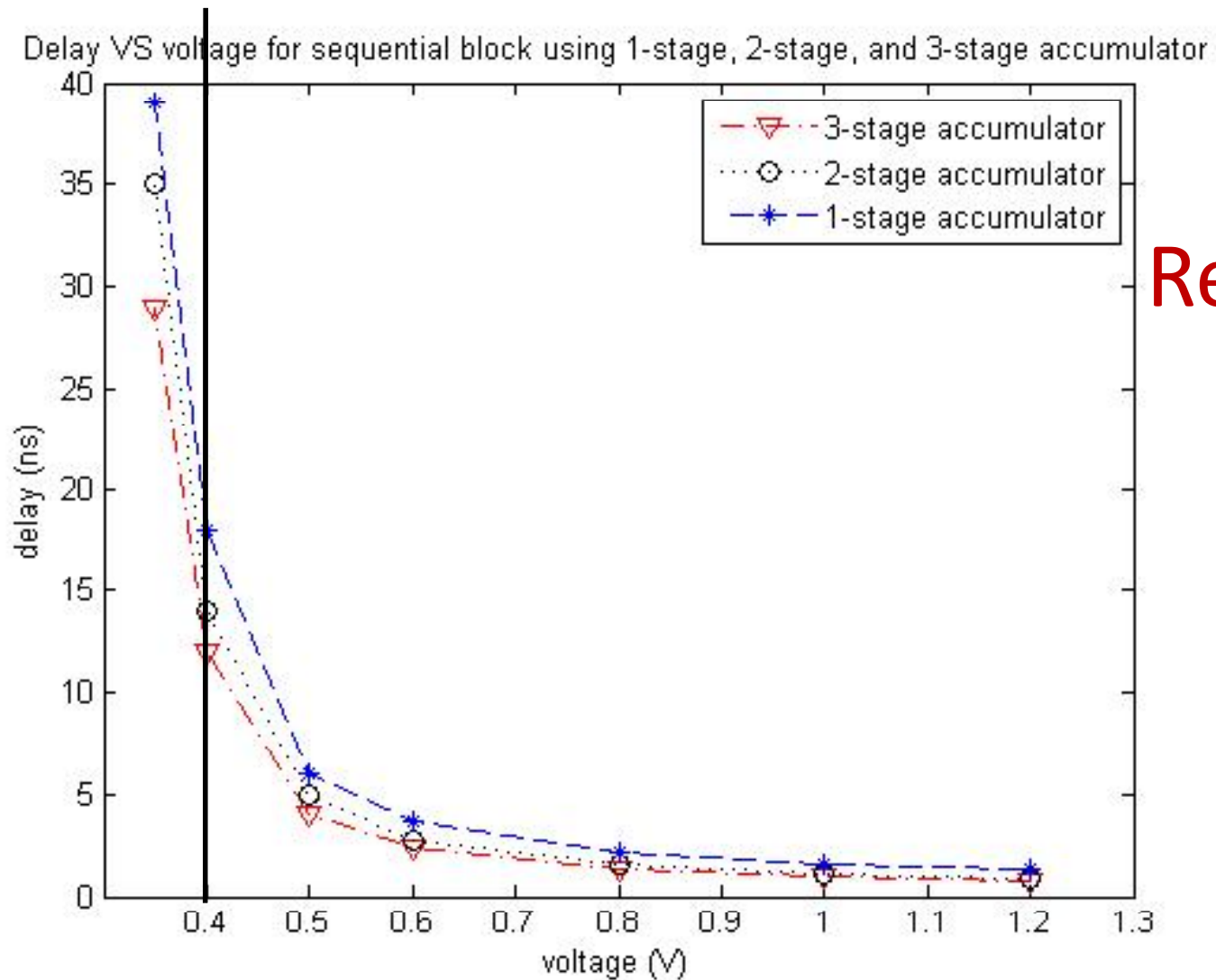


Reliability




Parallel Implementation

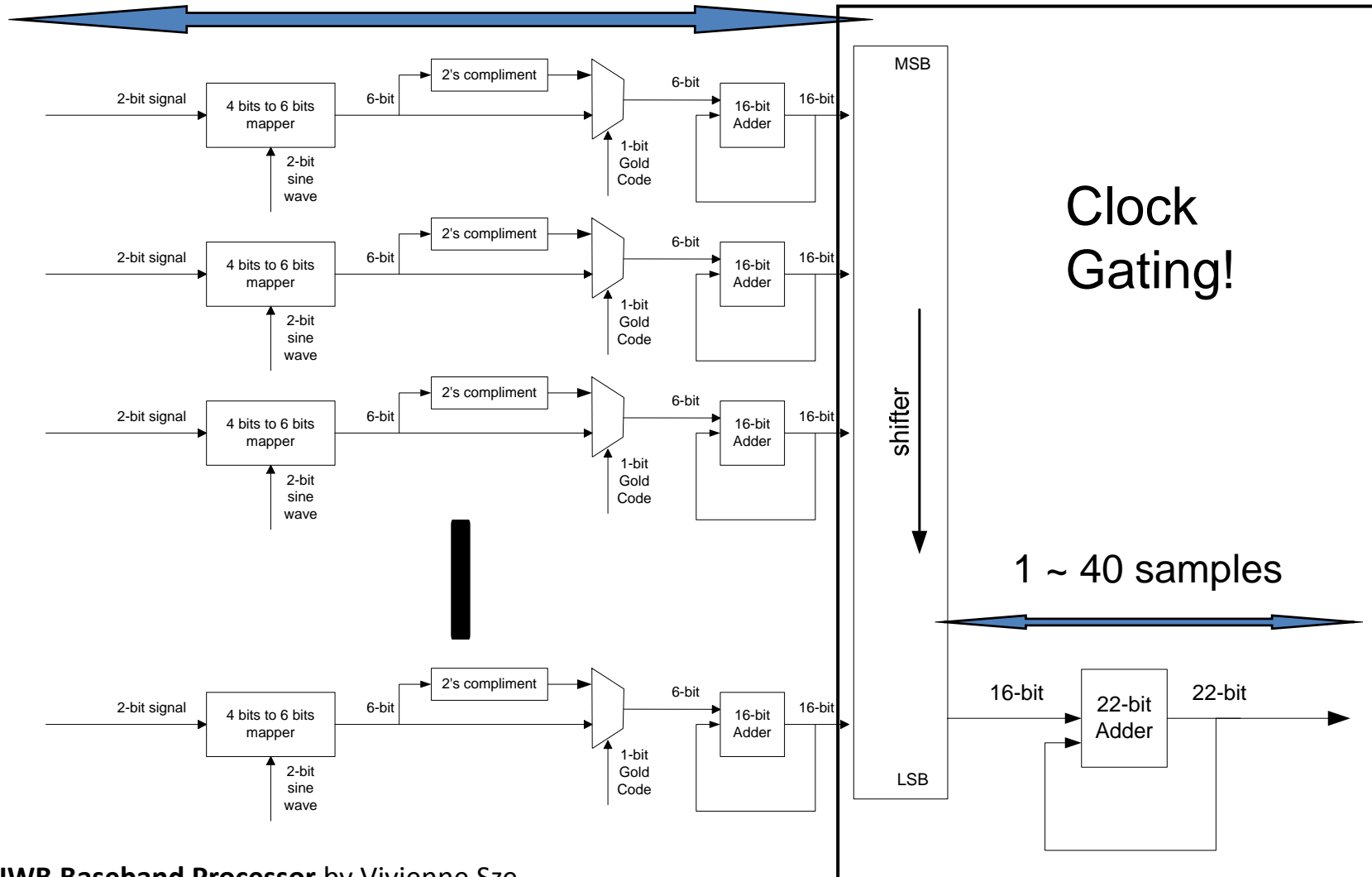
1ms, or 1023 chips, or 40,960 samples, or 409,600 samples



Estimation of Power Consumption

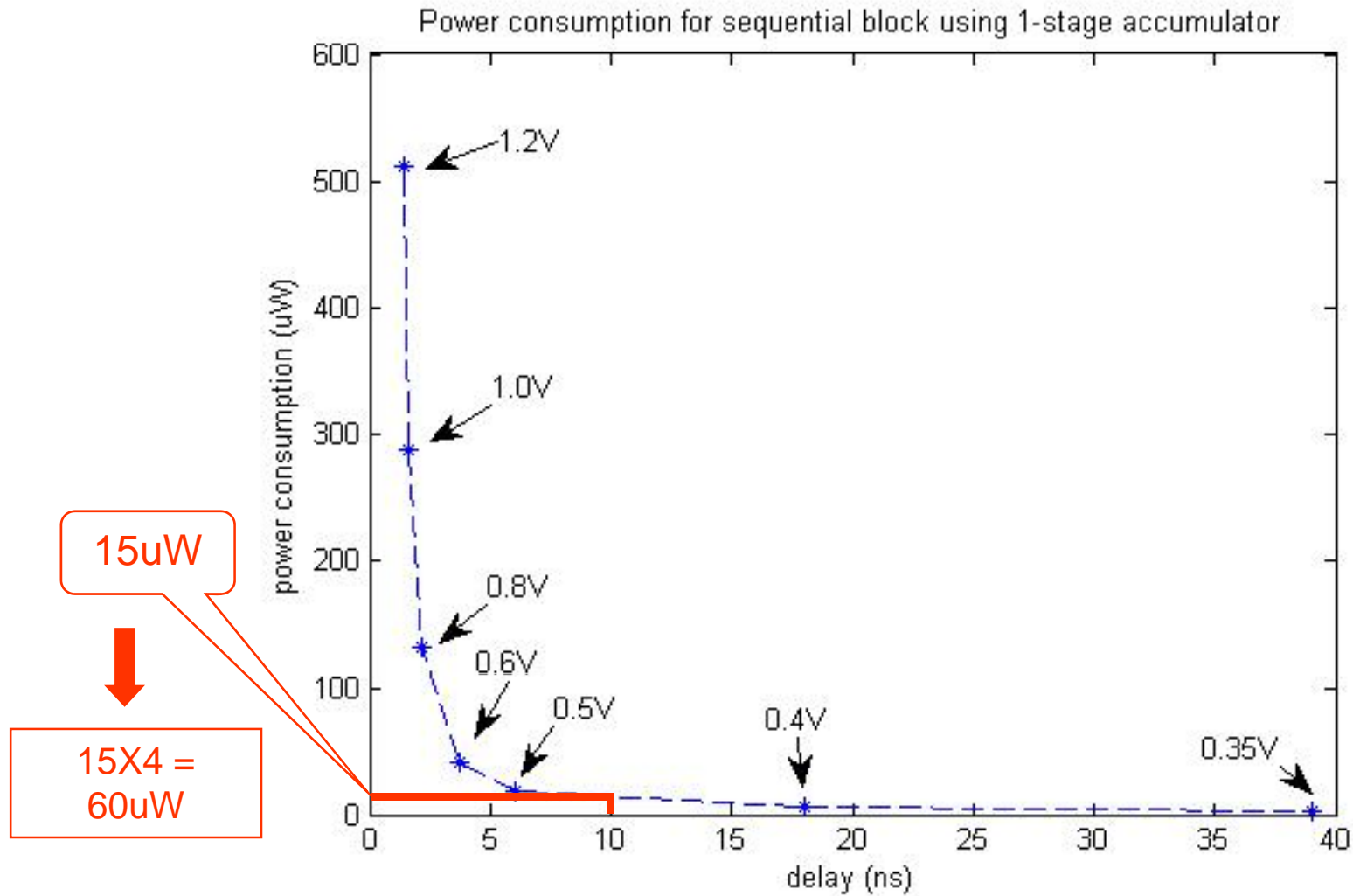

Power Consumption for 400MHz Receiver

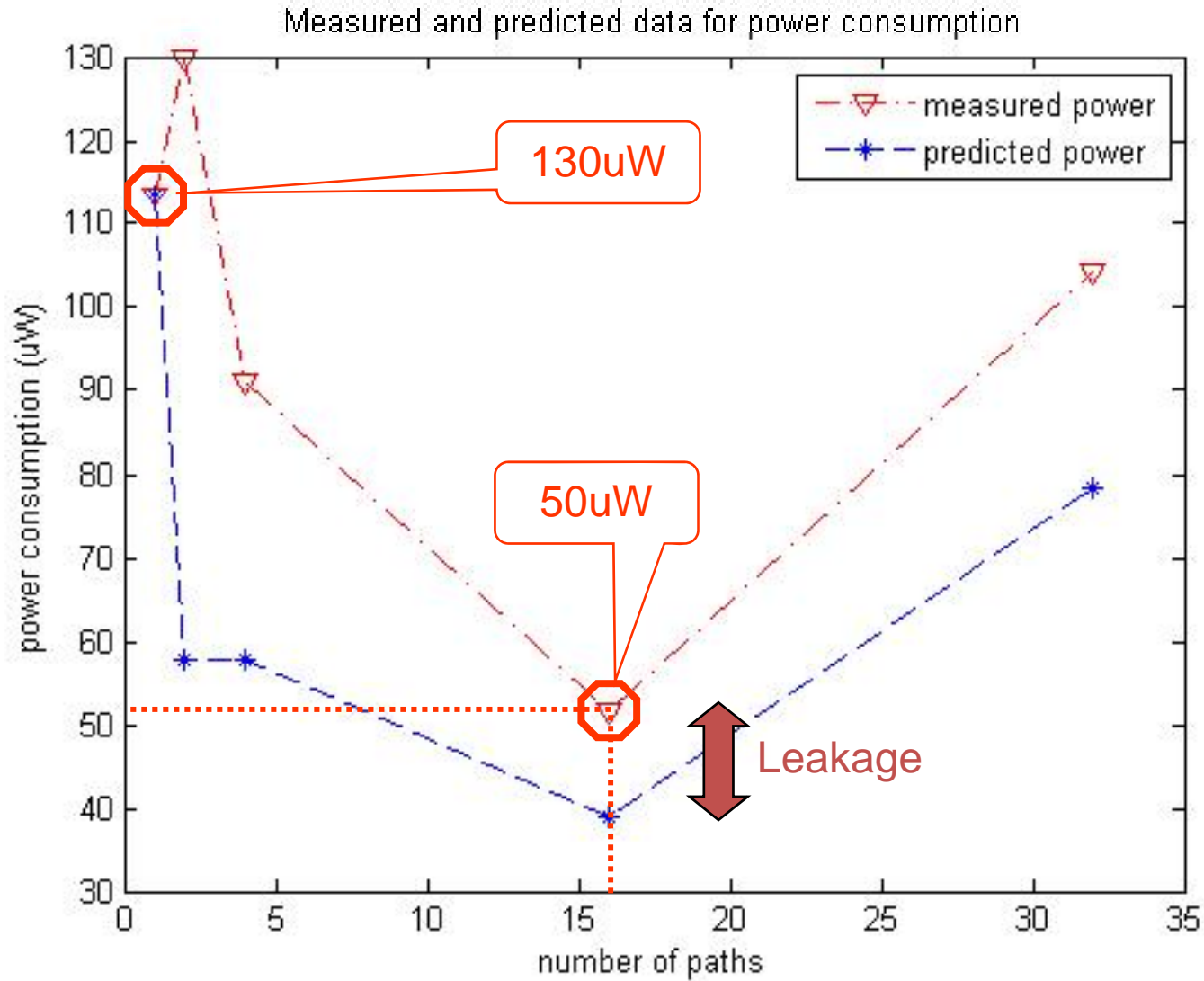

Conclusion

40MHz -- pipelining

400MHz -- parallelism

Future Work

- Leakage Problem
- Power gating to shifter and 2nd accumulator
- Layout
- Assistant circuit blocks
 - Harmonic wave generator
 - Gold code generator
- Better power v.s path plot